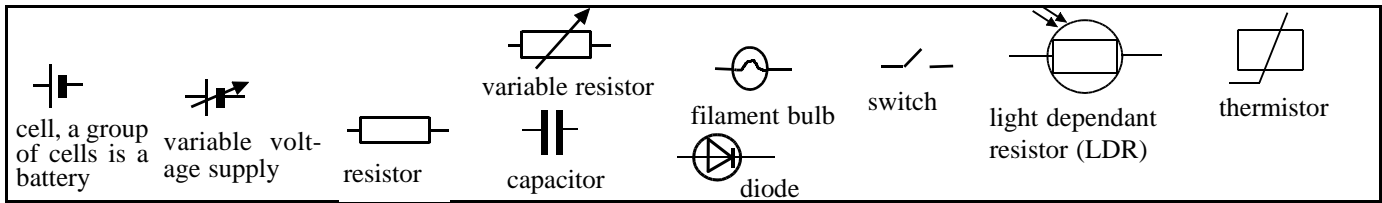


P6 ELECTRICITY FOR GADGETS

written by MJ Bradley



Current Electric current is the drift of charge through a conductor. In metals the charge is made of free electrons and it is negative. In liquids charge is made of positive or negative ions


quantity	symbol	unit	symbol
current	I	amp	A
voltage (pd)	V	volt	V
resistance	R	ohm	

Resistance.

Nearly everything resists the flow of electric current. Good electric conductors have low resistance and current can be high. Insulators have a high resistance and current through them is low.


resistance = voltage / current

$R = V/I$

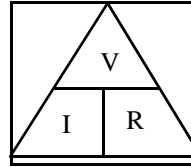

Example (1) What is current through a 2Ω resistor if the pd is 6V?
answer: $I = V/R = 6/2 = 3A$

Current-Voltage graphs

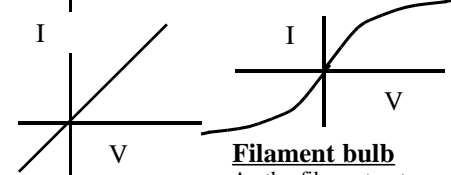


Ohmic resistor

Current is proportional to voltage and resistance ($R=V/I$) is constant

Filament bulb

As the filament gets hotter its resistance increases and current is no longer proportional to voltage

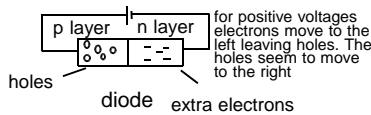The diode has very large resistance for negative voltages. At $+0.6V$ resistance drops dramatically. Diodes permit current in one direction only



Thermistor and Light dependant Resistor(LDR)

A thermistor's resistance drops with increasing temperature




The resistance of an LDR drops with increased light




Variable Resistors:

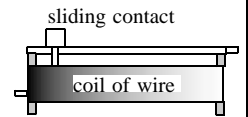These work by a sliding contact moving along a resistance wire. The longer the wire the greater the resistance




Generating Electricity

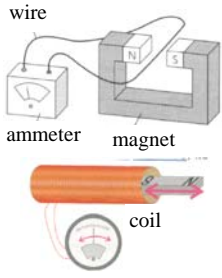If a wire is moved through a magnetic field current is produced. The same effect can be achieved by using a coil of wire and moving the magnet in and out of the coil. The current is increased by moving the magnet faster, a stronger magnet, or more turns of wire in the coil. If the magnet is reversed the current direction reverses



A.C. generator

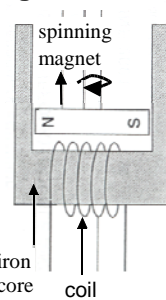


In this generator the magnet spins and because the field direction constantly reverses so does the current direction. Alternating current (a.c.) is produced



Transformers are used to step up the voltage at power stations and to step down voltage near our homes in a sub-station. Transformers only work with A.C.

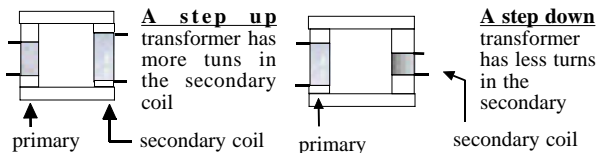How do they work? The alternating current delivered to the primary produces an alternating magnetic field which cuts across the secondary coil and a voltage is produced. Direct current (d.c) would not work because the current is steady and the magnetic field stationary.



The output voltage is related to the ratio of the number of turns in the primary and secondary coils

$$\frac{\text{secondary voltage}}{\text{primary voltage}} = \frac{N^{\circ} \text{ of turns in secondary}}{N^{\circ} \text{ of turns in primary}} \quad \frac{V_s}{V_p} = \frac{N_s}{N_p}$$

Example What is the secondary voltage from a transformer if the input voltage is 10V, there are 100 turns in the primary and 1000 turns in the secondary?


answer $V_s = \frac{N_s}{N_p} \times V_p = \frac{1000}{100} \times 10 = 100V$

This is a step up transformer

Transformer Efficiency If energy losses are ignored power to primary = power output from secondary

$$I_p V_p = I_s V_s \text{ so } V_s = \frac{I_p V_p}{I_s}$$

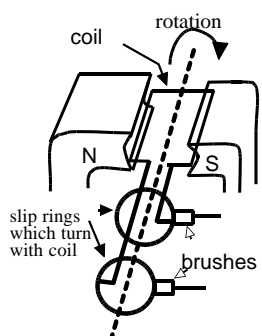
Transporting Electricity: Energy loss is proportional to the square of the current flowing. if V_s is made very high I_s is small and so energy loss is reduced



In this A.C. generator a coil rotates in a magnetic field. The coil is attached to slip rings which rub against contacts (brushes). The coil has to be made to rotate

Potential Divider (sharing voltage)

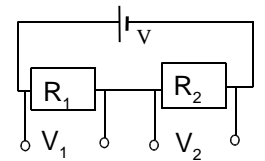
In a series circuit voltage is shared across the resistors.



The amount of the share is calculated by these equations. A potential divider can control voltage in a circuit

$$V_1 = \frac{V R_1}{R_1 + R_2} \quad V_2 = \frac{V R_2}{R_1 + R_2}$$


Examples of Potential Divider Circuits

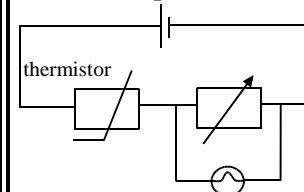

As the temperature increases the thermistor resistance drops and so does its share of the voltage. There is more voltage across the resistor and the bulb gets brighter


What would be the effect of increasing the resistance? answer: The bulb will switch on at a lower temperature.

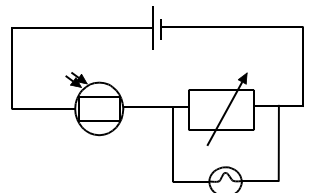In this circuit as it gets brighter the resistance of the LDR decreases, its share of the voltage decreases. There is now more voltage across the variable resistor and the bulb turns on




What would be the effect of increasing the resistance? ans: It would not need to get as bright before the bulb lights

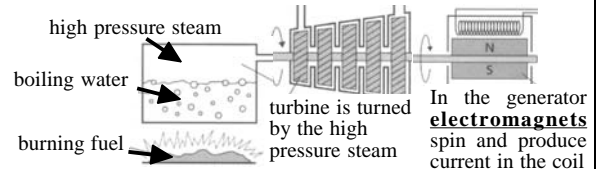Generating Electricity at a Power Station




In the generator **electromagnets** spin and produce current in the coil

Electric Current and Magnetism

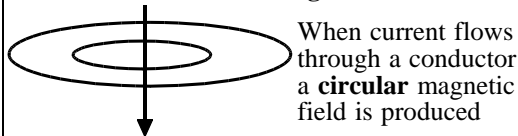


When current flows through a conductor a **circular** magnetic field is produced

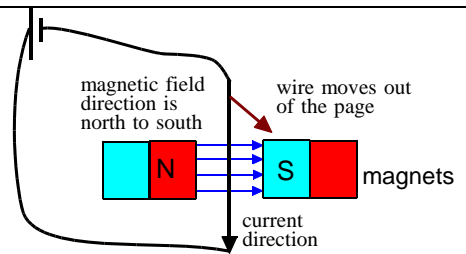The Motor Effect If current passes through a wire the magnetic field that is produced around it can interact with the permanent magnetic field from a magnet and the wire experiences a force. If the current is reversed so is the force. Alternating current would make the wire move forwards and backwards




Alternating Current and Direct Current

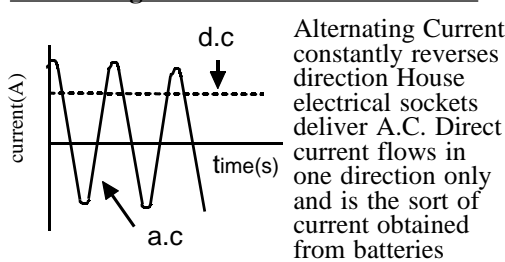

Alternating Current constantly reverses direction House electrical sockets deliver A.C. Direct current flows in one direction only and is the sort of current obtained from batteries

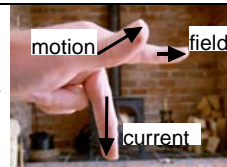Flemmings Left Hand Rule Place your thumb and first two fingers at **right angles**. Place your first finger in the direction of the field and your second finger in the direction of the current. Your thumb gives you the direction of movement




Converting a.c to d.c


Devices that work off batteries like your mobile phone use d.c. To charge a mobiles' battery mains a.c needs to be **rectified** (changed) to d.c

Diodes: These allow current to flow in one direction only - great for converting a.c. to d.c.


Half wave rectification

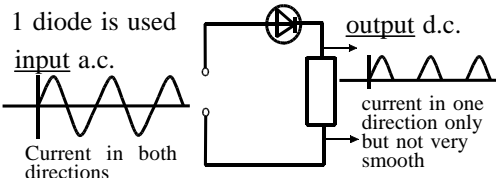

Full wave rectification

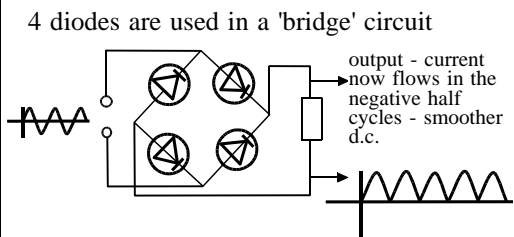


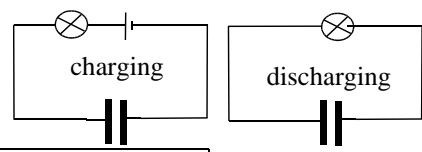Capacitors: These store charge. When they discharge current flows




When charging the current quickly drops. At full charge the current is zero and the voltage is maximum

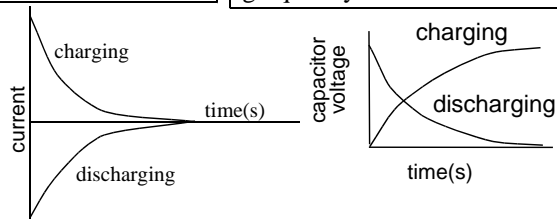
With the voltage supply removed the capacitor discharges and current flows in the opposite direction. The current and the capacitor voltage quickly reduces to zero



Smoothing d.c. in rectifier circuits

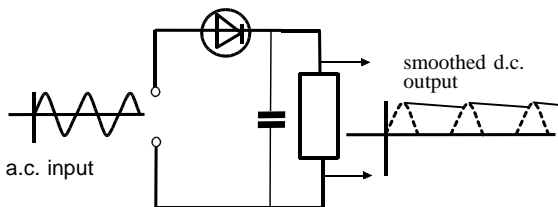


The Electric Motor

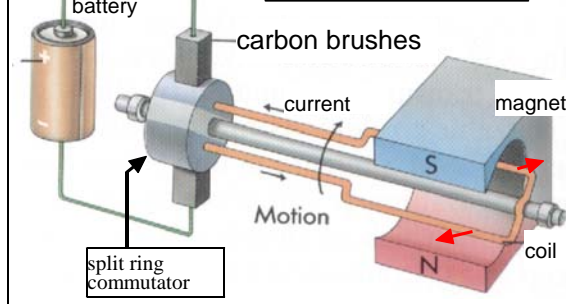

Current from the battery enters the coil via a carbon brush and the split ring commutator. The sides of the coil experience force in opposite directions because the current is flowing in opposite directions and the coil spins on its axis. Use the left hand rule to check this out for yourself

Electronic Circuits

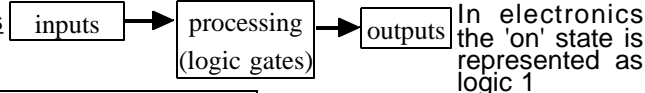

In electronics the 'on' state is represented as logic 1

NOT gate A \rightarrow B

input A	output B
1	0
0	1

The not gate reverses logic

AND gate A B \rightarrow C

input A	input B	output C
1	0	0
0	1	0
0	0	0
1	1	1

OR gate A B \rightarrow C

input A	input B	output C
1	0	1
0	1	1
0	0	0
1	1	1


NOR gate

This is an OR gate followed by a NOT

NAND gate

This is an AND gate followed by a NOT

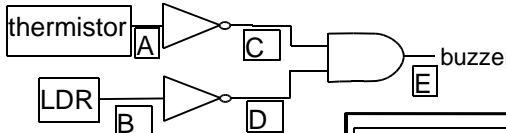Circuit Problem Example: A gardener wants a buzzer to sound if it is night time and it is freezing outside




input/output	logic 1	logic 0
switch	on	off
thermistor	hot	cold
LDR	bright	dark
bulb	on	off
buzzer	on	off

Truth table

input A	input B	C	D	output E
1	0	0	1	0
0	1	1	0	0
1	1	0	0	0
0	0	1	1	1

Potential Dividers and Logic

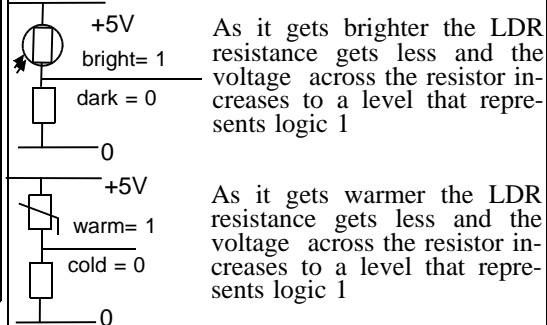

When the voltage is positive the current can flow and the capacitor also charges. When the voltage is negative no current can flow back through the diode. Instead the capacitor discharges through the resistor helping to maintain the current


What is a relay? This is a switch which uses a small current to switch on a bigger current in a separate circuit. This makes it safer to operate and saves the need for lots of thick wiring

REVISION EXERCISE UNIT P6


fold along dotted line

written by MJ Bradley

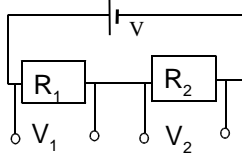
- 1) Draw the circuit symbol for (a) thermistor, (b) light dependant resistor,
- 2) Resistance = $\frac{?}{?}$ $R = \frac{?}{?}$
- 3) A resistor passes a current of 3A when the potential difference is 30V. What is the resistance? [4]
- 4) What current will flow through a 10W resistor when the voltage is 4V?
- 5) A diode permits current flow in _____ direction
- 6) A thermistors resistance _____ as the temperature gets higher
- 7) The resistance of a LDR _____ as light levels increase
- 8) A potential divider splits _____
- 9) Use the correct symbols to write an equation for (a) V_1 , (b) V_2
- 9c) What will happen to voltage V_2 if resistance R_1 is increased?



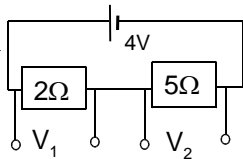
- 10) In this potential divider circuit what is (a) V_1 , (b) V_2 ?



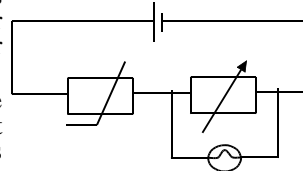
- 11) When it is hot the thermistor resistance is low, the voltage share across the thermistor gets _____ and across the variable resistor gets _____ and the bulb gets _____. As it gets colder the thermistor resistance increases and the voltage across it _____. At the same time the share of the voltage across the variable resistor gets _____ and the bulb goes _____. If resistance from the variable resistor is increased the bulb will light at a _____ temperature



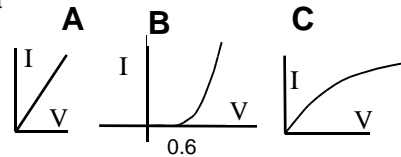
- 12) Match the current voltage graph to the correct circuit component
filament bulb, diode, ohmic resistor



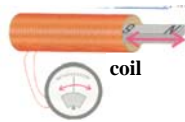
- 13) For negative voltages a diodes resistance is very _____
- 14) For an ohmic resistor current is _____ to voltage (at steady temperature)
- 15) Why is current not proportional to voltage in a filament lamp?
- 16) To generate current the magnet must be _____. The magnetic _____ around the magnet cuts across the coils and current is produced. The current can be increased by moving the magnet _____ or by having a _____ magnet or by having _____ turns in the coil. The current direction is reversed by



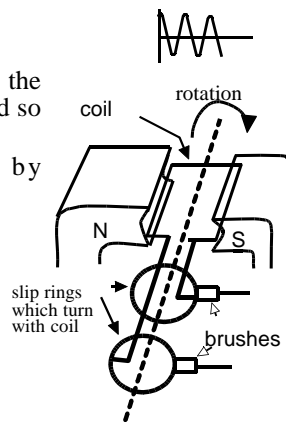- 17) What type of current does this graph represent?
- 18) In this a.c. generator after half a turn the side of the coil which **was** moving up is **now** moving _____ and so the current direction is _____.
- 18b) The current could be increased by



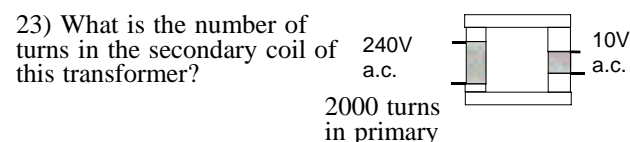- 19) A step up transformer _____ voltage and has _____ turns in the _____ coil than in the primary coil
- 20) A step down transformer _____ voltage and has _____ turns in the secondary than in the primary coil
- 21) A transformer changes voltage in proportion to the change in the number of _____ in the primary and secondary
- 22) The transformer equation is?



- 1a)
- 1b)
- 2) resistance = $\frac{\text{voltage}}{\text{current}}$ $R = \frac{V}{I}$
- 3) $R = V/I = 30/3 = 10\Omega$
- 4) $I = V/R = 4/10 = 0.4 \text{ A}$
- 5) One
- 6) drops
- 7) drops
- 8) voltage

- 9a) $V_1 = \frac{VR_1}{(R_1+R_2)}$ 9b) $V_2 = \frac{VR_2}{(R_1+R_2)}$
- 9c) It will get less (look at the equation)

- 10a) $V_1 = \frac{4 \times 2}{(2+5)} = \frac{8}{7} = 1.14\text{V}$
- 10b) $V_2 = \frac{4 \times 5}{(5+2)} = \frac{20}{7} = 2.86\text{V}$

- 11) less, more, brighter
increases, less, dim

lower

- 12) **A** - ohmic resistor **B** - diode
C - filament bulb

- 13) High
- 14) proportional
- 15) resistance increases as it gets hotter

- 16) moving, field
faster, stronger, more
moving the magnet in the opposite direction

- 17) a.c.

- 18) up, reversed
- 18b) spinning the coil faster or stronger magnet or more turns in the coil

- 19) increases, more, secondary

- 20) reduces, less

- 21) turns

$$22) \frac{V_s}{V_p} = \frac{N_s}{N_p}$$


$$23) N_s = N_p \frac{V_s}{V_p} = \frac{2000 \times 10}{240} = 83 \text{ turns}$$


REVISION EXERCISE UNIT P6

fold along dotted line


written by MJ Bradley

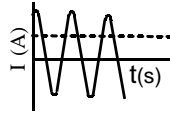- 24) Label the diagram with a.c. and d.c.
 25) What type of current do transformers use?




- 26) What is this circuit symbol? 
 27) In how many directions does a.c. flow?
 28) In how many directions does d.c. flow?
 29) Why is a diode useful for converting a.c. into d.c.?

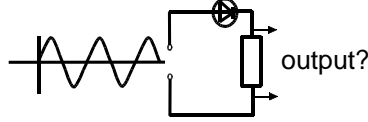30) a.c. is supplied to this diode and resistor. Sketch the output current




- 30b) What type of rectifier circuit is this?
 31) What type of a.c. to d.c. rectifier circuit uses 4 diodes?

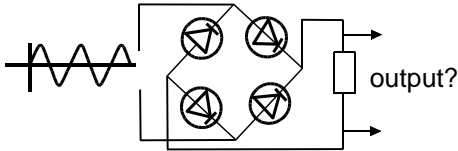31b) Sketch the output from this circuit when it is supplied with a.c.




- 32) What does a capacitor store?
 33) What flows when a capacitor discharges?

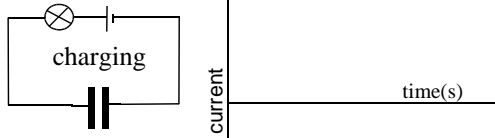34) A capacitor can be charged using this circuit. Sketch how current changes with time when the battery connection is made




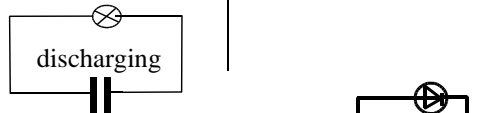34b) On the same graph sketch how current from the capacitor changes when it is discharged



35) In an a.c. to d.c. rectifier circuit d.c. can be smoothed using a _____. When the voltage is negative the capacitor _____ maintaining the _____

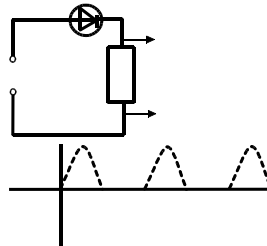36) Sketch how half wave rectified d.c. is smoothed when a capacitor is used



- 37) What type of field surrounds a wire carrying a current?
 37b) What shape is this field?

38) Why does this wire move when a current flows?

- 39) What rule enables the direction of movement to be predicted?
 40) Draw an arrow from the wire showing its direction of movement

41) In an electric motor How can the coil be made to spin faster?

42) In electronic 'on' is logic ___ and 'off' logic ___

43) A ___ gate reverses logic

44) Which gate has an output of logic 1 if both inputs are logic 1?


45) When does an OR gate give an output of logic 1?

46) Identify and label each logic gate



47) Complete the truth table for the circuit below

warm - logic 1
 cold - logic 0

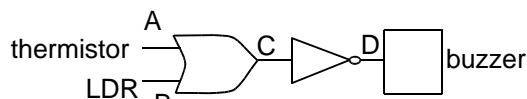

bright - logic 1
 dark - logic 0

A	B	C	D
1	0		
1	0		
0	0		
1	1		

47b) In what conditions will the buzzer sound?

47c) What type of gate does this circuit represent?

48) What is a NAND gate?

49) A _____ can be used to provide the logic 1 and 0 for logic gates.

50) What is the symbol for a NOR gate?

24)

25) a.c.


26) diode

27) two

28) one

29) It allows current to flow in one direction only


30)

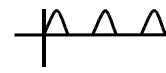

30b) Half wave

31) full wave


31b)

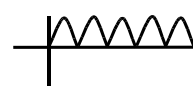

32) charge


33) current

34+34b

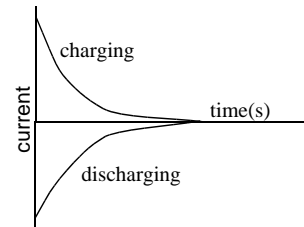

35) capacitor, discharges, current

36)

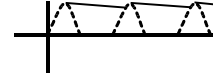

37) magnetic

37b) circular

38) magnetic field from wire interacts with field from magnets

39) Flemmings left hand rule

40) arrow from wire into the page

41) more current, stronger magnets, more turns

42) 1, 0

43) NOT

44) AND

45) When either input is logic 1

46) NOT

OR

AND

47)

A	B	C	D
1	0	1	0
1	0	1	0
0	0	0	1
1	1	1	0

47b) cold and dark

47c) NOR

48) AND gate followed by a NOT


49) potential divider

50)



UNIT P6 ASSESSMENT

NAME _____

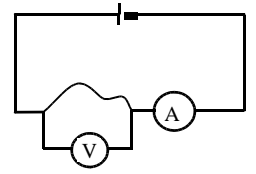


1(a) Dave builds a circuit. He uses a piece of resistance wire. Look at the diagram.

(i) The current in the wire is 0.2 amps. The voltage across the wire is 12V. Calculate the **resistance** of the wire. _____

[2]

(ii) Dave leaves the circuit connected and takes some more readings. The wire gets hot. Look at the graph of his results. Describe and explain the shape of this graph. Use ideas about **resistance** in your answer.


 _____ [3]

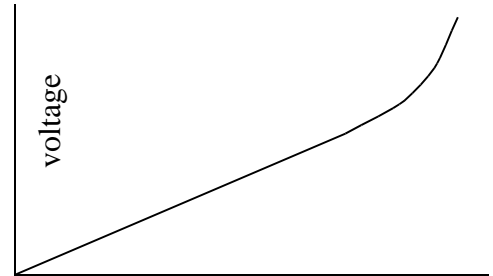

(b) Dave puts a motor and a **thermistor** in a circuit. Look at the diagram. Dave makes the thermistor **hotter** using the hair dryer.

(i) What happens to the **speed** of the motor? _____ [1]

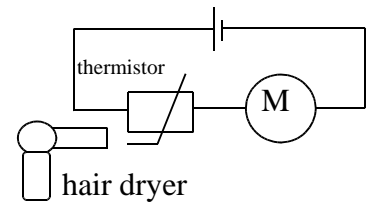
(ii) Explain your answer. _____
 _____ [1]



(c) Dave replaces the thermistor with a light dependent resistor (LDR) in his motor circuit. Look at the diagram. Dave switches on the lamp. More light hits the LDR.

(i) What happens to the **speed** of the motor? _____ [1]

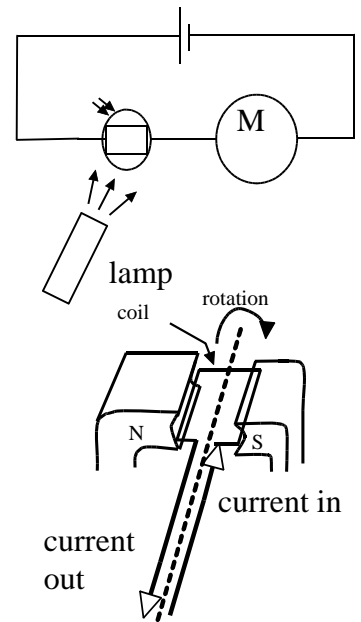(ii) Explain your answer. _____
 _____ [1]




2 This question is about electric motors.

Look at the diagram of the simple DC electric motor. A current flows through the coils. The motor spins. Alex wants to make the coil spin **faster**. Explain how he can do this.

In your answer write about: (i) **current**, (ii) **coils**, (iii) **magnetism**.

 _____ [3]

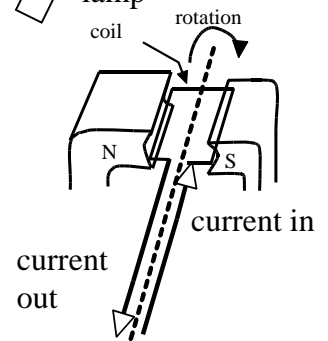

3 This question is about power generation and electrical transformers. The transformer increases the voltage from the power station to the transmission cables.



(a) There is a generator in the power station.

Look at the diagram of an AC generator. The coil spins and produces an output voltage.

(i) The coil spins **faster**. What happens to the **size** of the output voltage?

 What happens to the **frequency** of the output voltage?
 _____ [2]

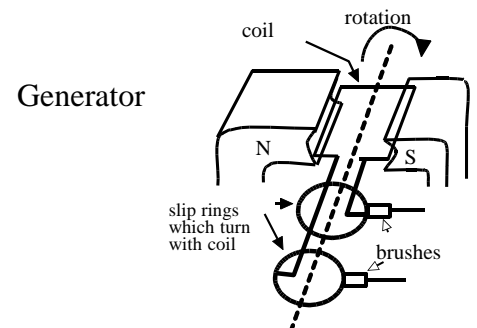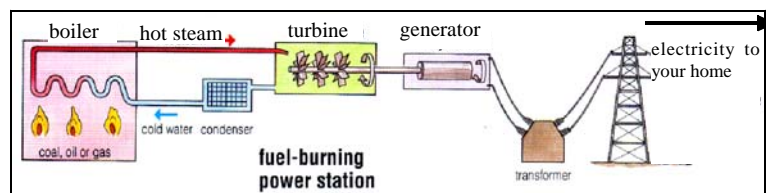(ii) The coil is replaced. The new coil has **more** turns. What happens to the size of the **output** voltage? _____ [1]




(b) Look at the diagram of the step-up transformer.

(i) The AC voltage produces a changing magnetic field in the primary coil. Explain how this produces an output voltage in the secondary coil. _____

_____ [2]

(ii) The input voltage is 20 000V. The primary coil has 3 000 turns. The output voltage is 400 000V. Calculate the number of turns in the secondary coil.

_____ [2]

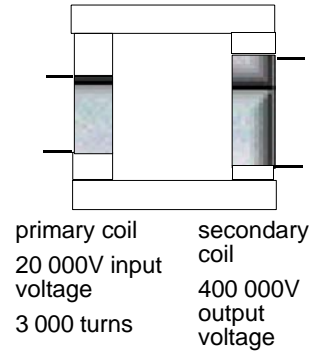


4 Alice measures the current and voltage for a diode. Look at the graph of her results.

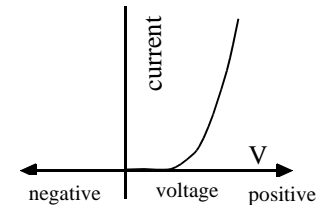(a) Complete the following sentences about this diode. Choose your answers from

forwards high low negative positive reverse

When the voltage is positive the resistance is _____ in the _____ direction. When the voltage is _____ the resistance is _____ in the **reverse** direction. [2]




(b) The diode is made of silicon. Look at the diagram

(i) The voltage is in the **forward** direction.

Explain what happens to the holes and electrons in the diode.

_____ [2]

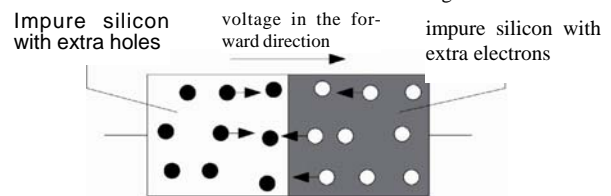

(ii) The voltage is changed to the **reverse** direction. Explain what happens to the holes and electrons in the diode.

_____ [2]

5) This question is about logic gates.

(a) Complete the outputs for the OR gate


(b) Complete the outputs for the AND gate [2]

OR gate		input A	input B	output C
A		1	0	
		0	1	
		0	0	
		1	1	

AND gate		input A	input B	output C
A		1	0	
B		0	1	
		0	0	
		1	1	

(c) Logic gates have to be connected to a **relay** before they control mains circuits. Explain **two** reasons why a relay is needed. _____

_____ [2]

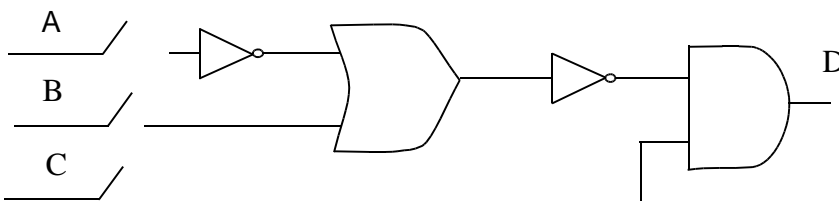

INPUT	on or off?
A	
B	off
C	

(d) Logic gates can be made to control a combination lock. Look at the diagram. It shows the three inputs to the lock. The lock will only open when there is a **high** output at D. What combination of inputs will open the lock?

Complete the table.

[1]